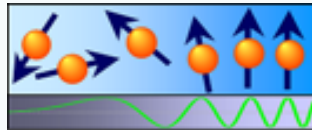


# Experimental Physics EP2a


## Electricity and Thermodynamics

**– Electric current –**  
**Ohm's law, power, circuits, Kirchoff's rules**




<https://bloch.physgeo.uni-leipzig.de/amr/>

# Electric current

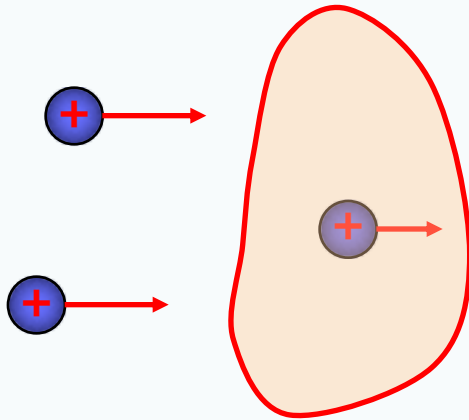

$$I_{av} = \frac{\Delta Q}{\Delta t} \quad I = \frac{dQ}{dt} \quad \left[ \frac{C}{s} \right] = [A]$$

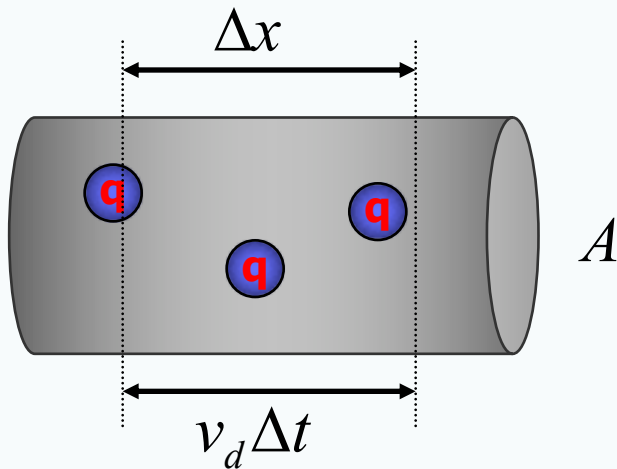**The direction of current is conventionally assumed to be opposite to the direction of flow of electrons.**




$$I_{av} = \frac{\Delta Q}{\Delta t} = \frac{nqAv_d\Delta t}{\Delta t} = nqAv_d$$

$$A = 3 \times 10^{-6} \text{ m}^2 \quad \rho_c = 8.95 \text{ g/cm}^3$$

$$M_c = 63.5 \text{ g/mol} \quad I = 10 \text{ A}$$

$$v_d \approx 2 \times 10^{-4} \text{ m/s}$$

# Drude's theory of electric conduction

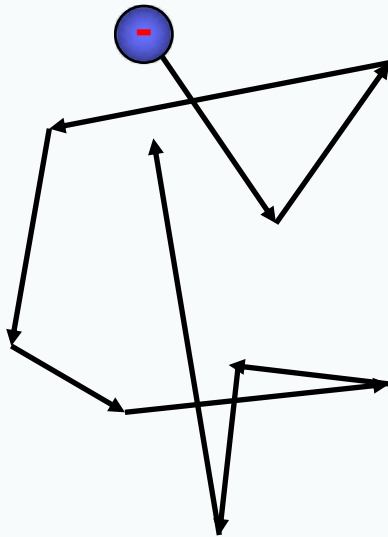


$$\vec{F} = q\vec{E} = m_e \vec{a}$$

$$\vec{v}_f = \vec{v}_i + \vec{a}t = \vec{v}_i + \frac{q\vec{E}}{m}t$$

$$\vec{v}_d = \frac{q\vec{E}}{m} \tau$$

← average time between collisions
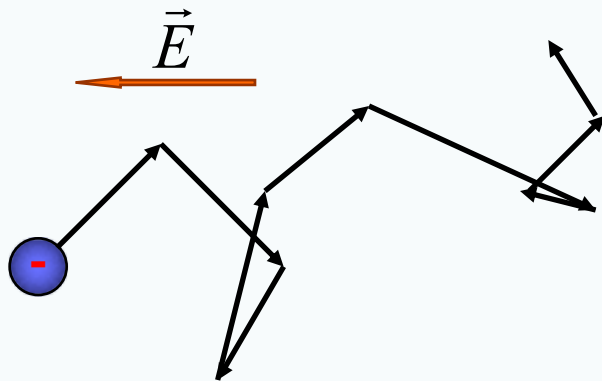
$$\vec{J} = nq\vec{v}_d \quad \vec{J} = \sigma \vec{E}$$



$$\vec{J} = nq^2 \frac{\vec{E}}{m_e} \tau$$

$$\tau = \frac{l}{\bar{v}}$$


# Ohm's law

$$\vec{J} \equiv \frac{\vec{I}}{A} = nq\vec{v}_d$$

$$\vec{J} = \sigma \vec{E}$$

$\sigma$  - conductivity

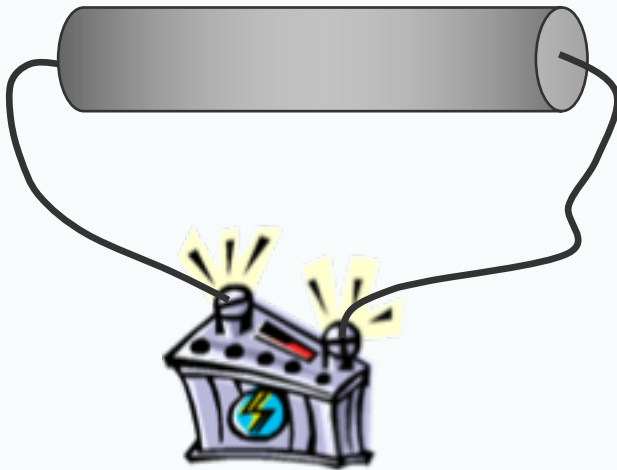Materials obeying this equation are *ohmic*.





$$\Delta V = E \cdot l = \frac{J \cdot l}{\sigma} = \frac{l}{A\sigma} I$$

$$R \equiv \frac{l}{A\sigma}$$






resistance  $[\Omega]$

$$\rho \equiv \frac{1}{\sigma} = R \frac{A}{l}$$



resistivity

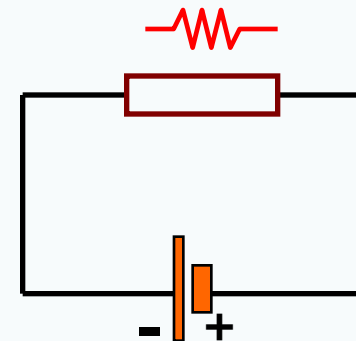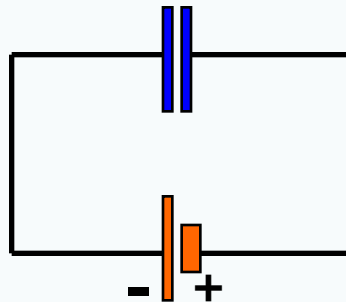

# Current-potential curve

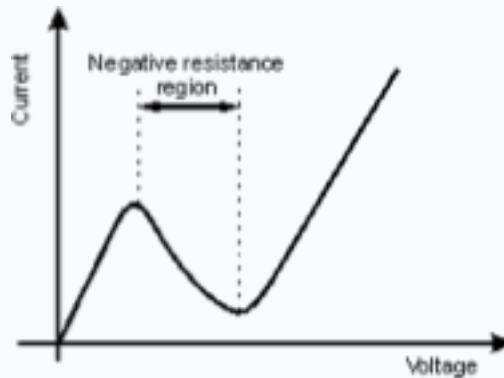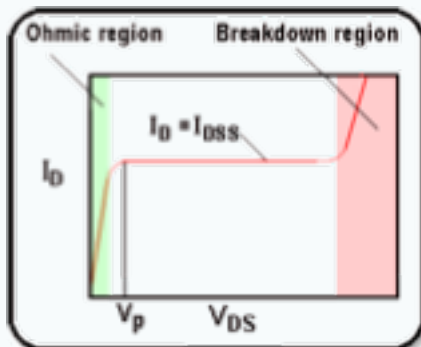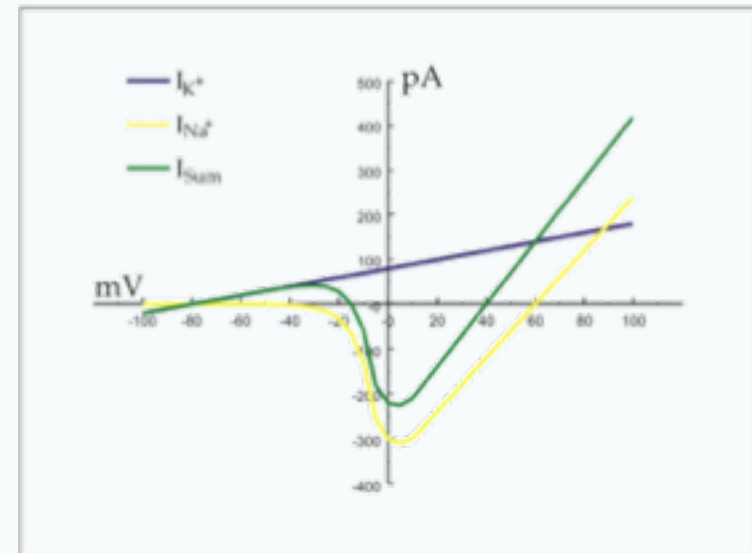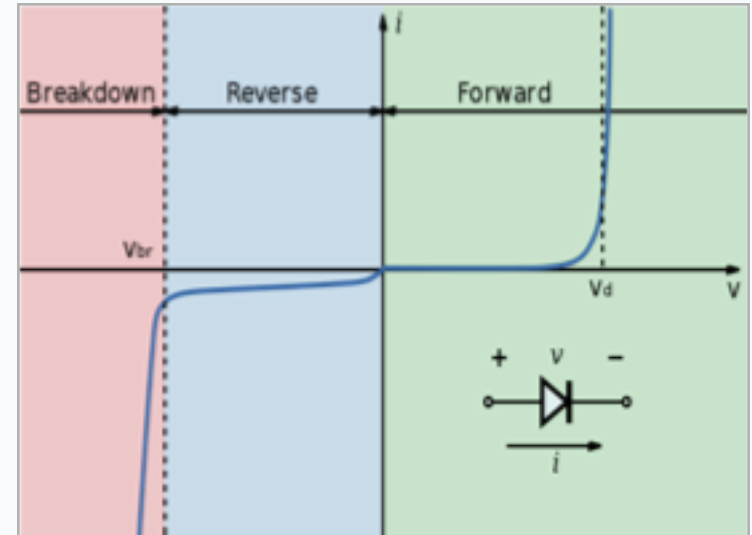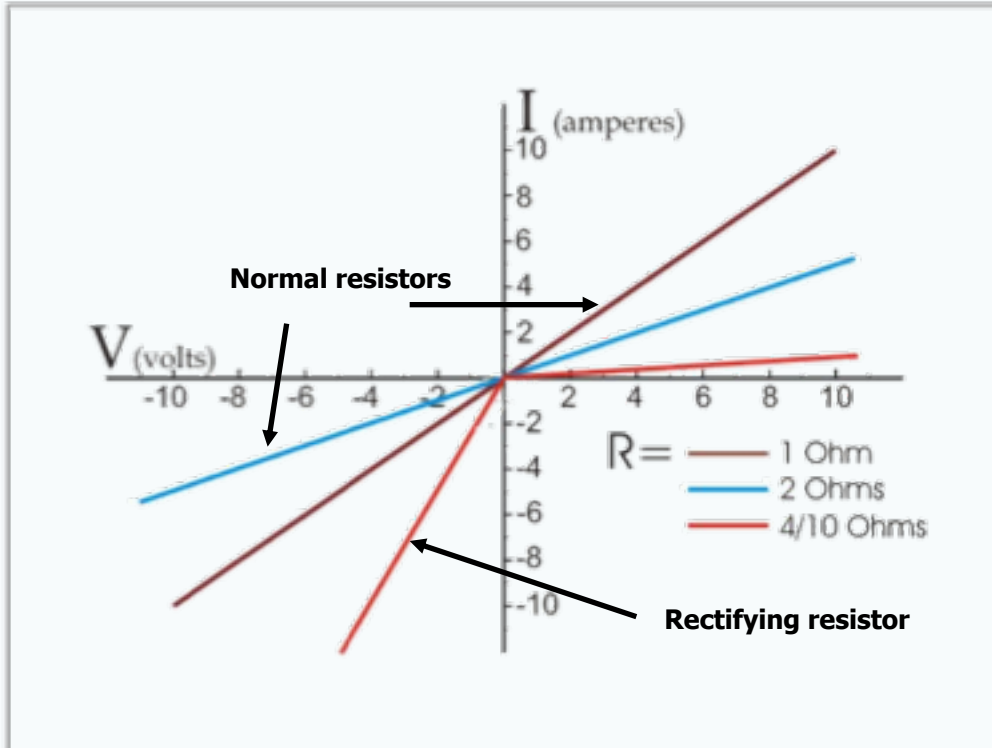


# Power

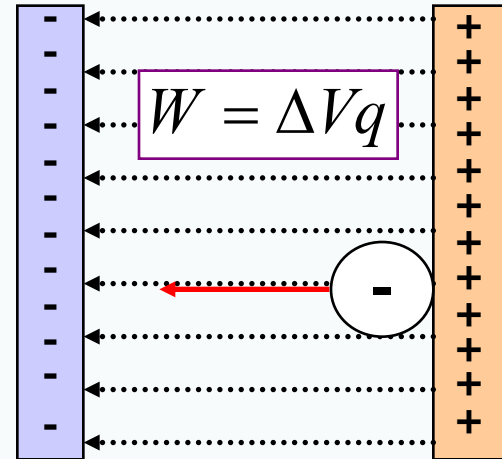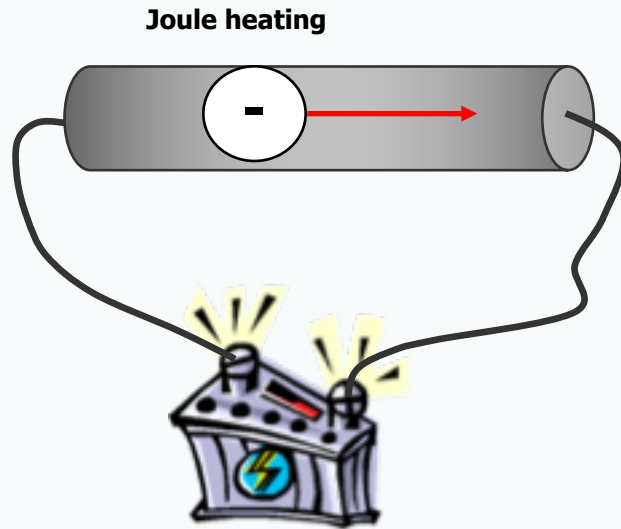

$$\frac{\Delta U}{\Delta t} = \frac{\Delta V \Delta Q}{\Delta t} = I \Delta V$$

$$P = I^2 R = \frac{(\Delta V)^2}{R}$$


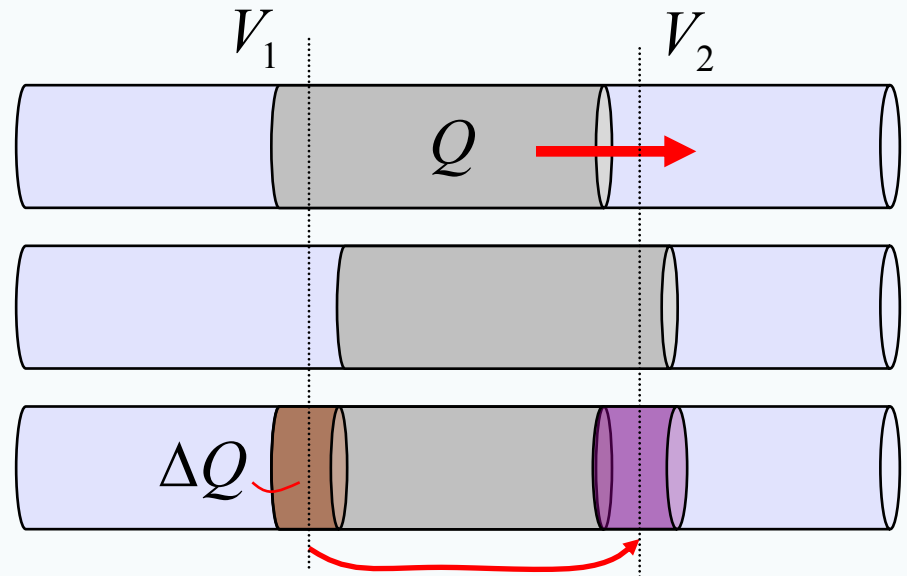


# Temperature coefficient of resistivity


$$R = \rho \frac{l}{A}$$

$$\rho = \rho_0(1 + \alpha(T - T_0))$$

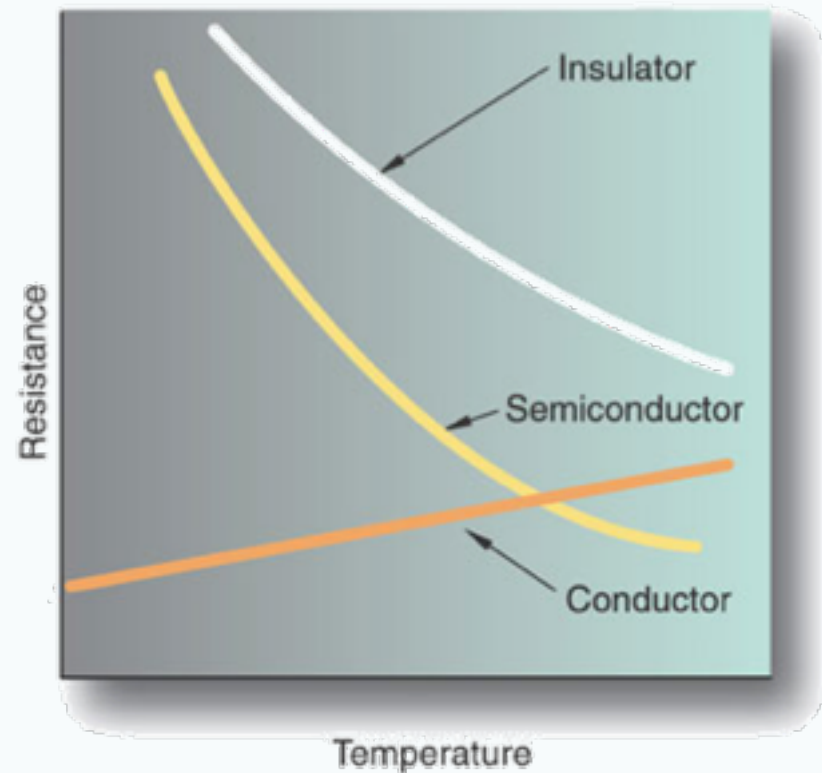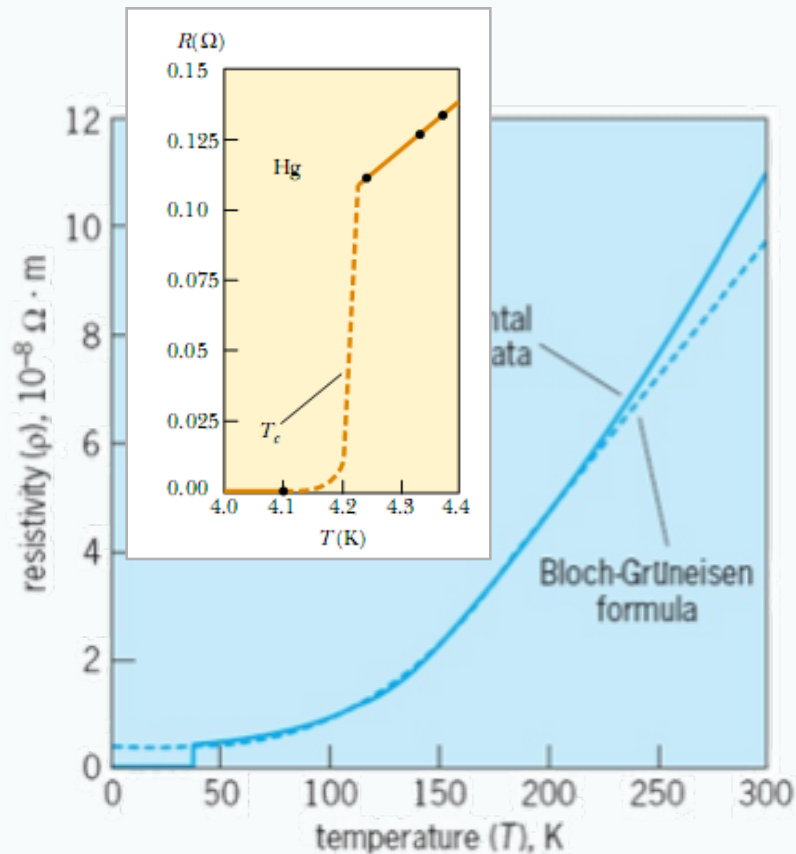
$$\alpha = \frac{1}{\rho_0} \frac{d\rho}{dT}$$



# Electromotive force

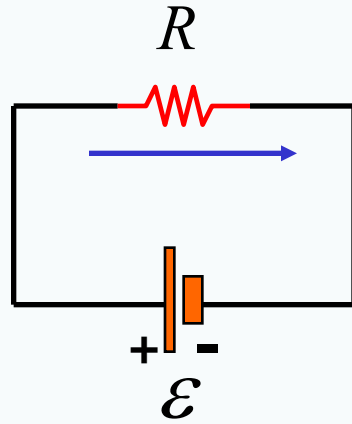


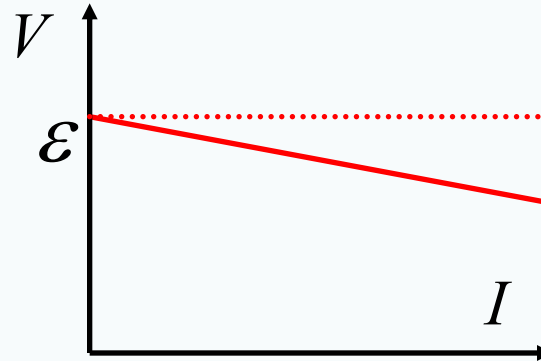
The work per unit charge is called the *emf* of the source.



$$\Delta V = \mathcal{E} - Ir$$


$$\Delta V = IR$$

$$I = \frac{\mathcal{E}}{R + r}$$

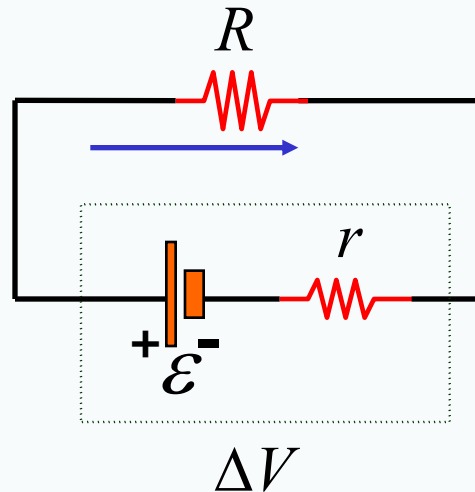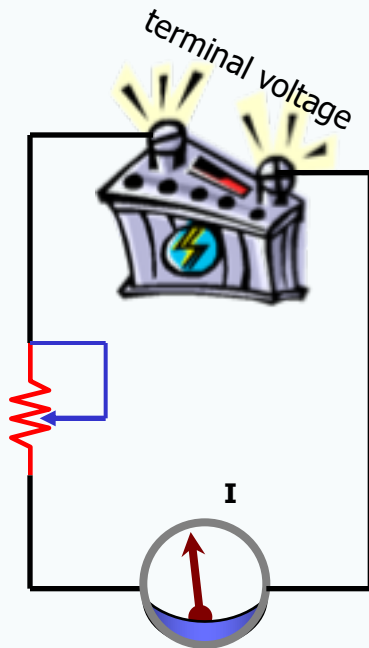



# Maximal power delivered

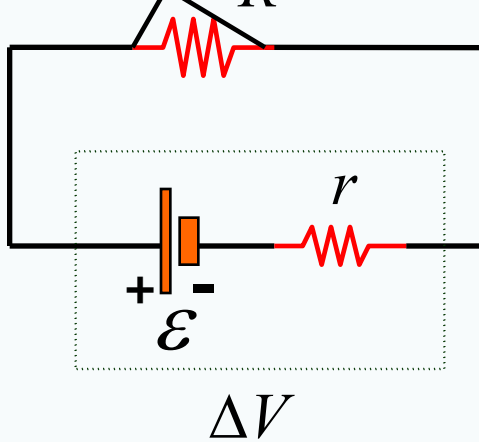

$$I = \frac{\mathcal{E}}{R + r}$$


$$P = I^2 R = \frac{\mathcal{E}^2 R}{(R + r)^2}$$

$$\frac{dP}{dR} = \frac{\mathcal{E}^2}{(R + r)^2} - 2 \frac{\mathcal{E}^2 R}{(R + r)^3} = 0$$


$$R = r$$
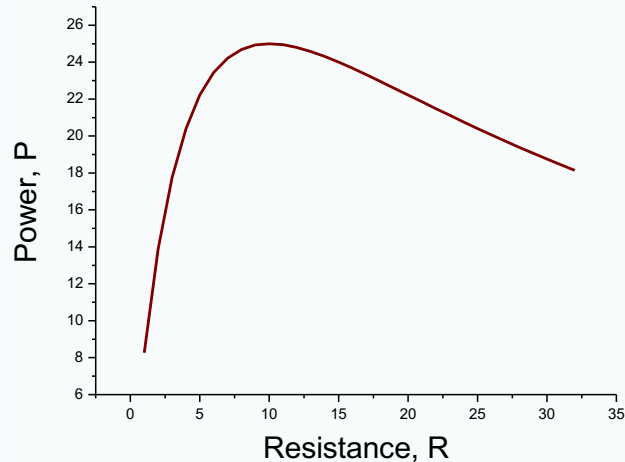
## Impedance matching

Choosing  $R = r$  to maximize the power delivered to the load resistor.




# Combination of resistors

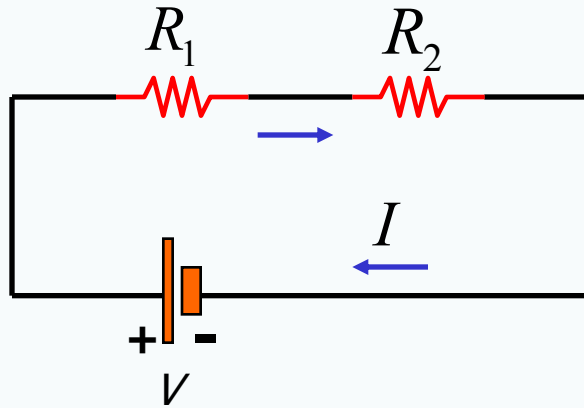

$$V = V_1 + V_2 = IR_1 + IR_2$$

$$R = R_1 + R_2$$

$$R_{ser} = \sum R_i$$

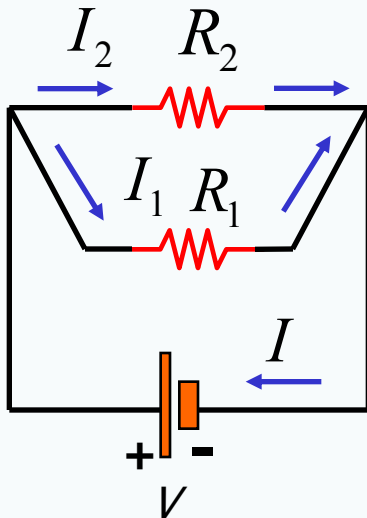

$$I = I_1 + I_2$$


$$V = I_1 R_1 = I_2 R_2$$

$$\frac{1}{R} = \frac{I}{V} = \frac{I_1 + I_2}{V} = \frac{V/R_1 + V/R_2}{V}$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$R_{\parallel}^{-1} = \sum R_i^{-1}$$

# Kirchhoff's rules

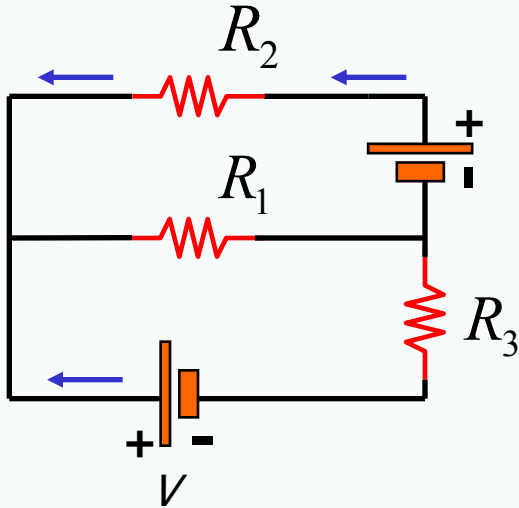

**When any closed loop is considered, the sum of the changes in electric potential must be zero.**

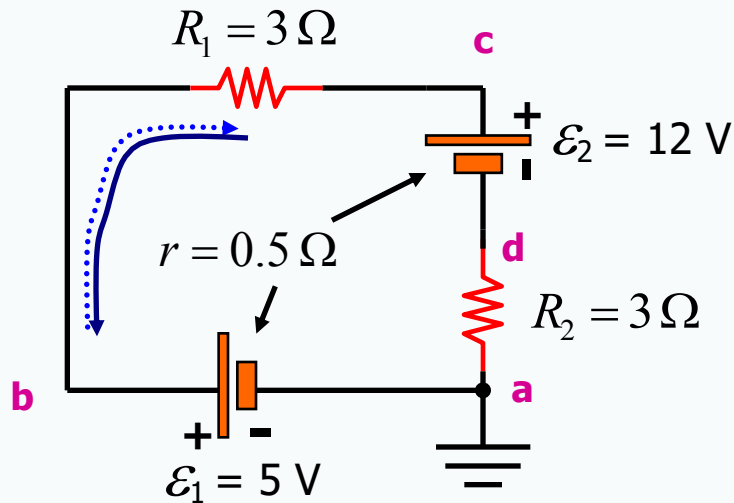**At any branching point the sum of all currents (incoming and outgoing) must be zero.**



$$\mathcal{E}_1 - Ir_1 - IR_1 - \mathcal{E}_2 - Ir_2 - IR_2 = 0$$

$$I = \frac{\mathcal{E}_1 - \mathcal{E}_2}{R_1 + R_2 + r_1 + r_2} = -1 \text{ A}$$


$$V_a = 0 \text{ V} \quad V_d = V_a - 1 \cdot 3 = -3 \text{ V}$$

$$V_c = V_d + 12 - 1 \cdot 0.5 = 8.5 \text{ V}$$

$$V_b = V_c - 1 \cdot 3 = 5.5 \text{ V}$$

$$V_a = V_b - 5 - 1 \cdot 0.5 = 0 \text{ V}$$

# Kirchhoff's rules

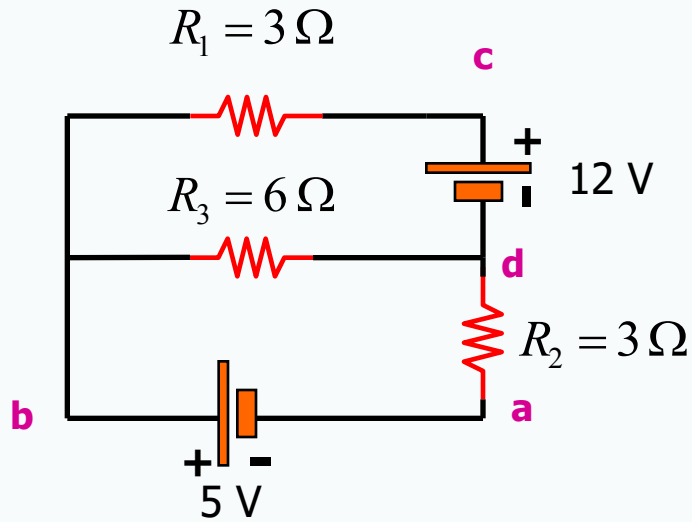

$$I_1 + I_2 - I_3 = 0$$

$$-I_1 R_1 - 12\text{ V} + I_2 R_3 = 0 \quad / 3\ \Omega$$

$$-I_1 - 4\text{ A} + 2I_2 = 0$$


$$-I_2 R_3 - I_3 R_2 + 5\text{ V} = 0$$

$$-6I_2 + 5\text{ A} - 3I_3 = 0$$

$$I_1 = -\frac{26}{15}\text{ A}$$

$$I_2 = \frac{17}{15}\text{ A}$$

$$I_3 = -\frac{9}{15}\text{ A}$$

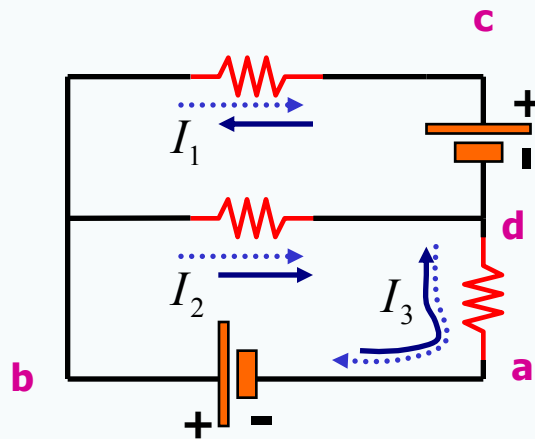

$$P_{R_2} = I_3^2 R_2 = \frac{81}{225} \cdot 3 = 1.08\text{ W}$$

$$W_{R_2} = P \Delta t = 5.4\text{ J}$$

$$P_{R_3} = 7.71\text{ W}$$


$$P_{R_1} = 9.01\text{ W}$$

$$\sum P_R = 17.8\text{ W}$$

$$P_{\varepsilon_{12}} = I_1 \cdot \varepsilon_{12} = 20.8\text{ W}$$

$$P_{\varepsilon_5} = I_3 \cdot \varepsilon_5 = 3\text{ W}$$

# Real life story

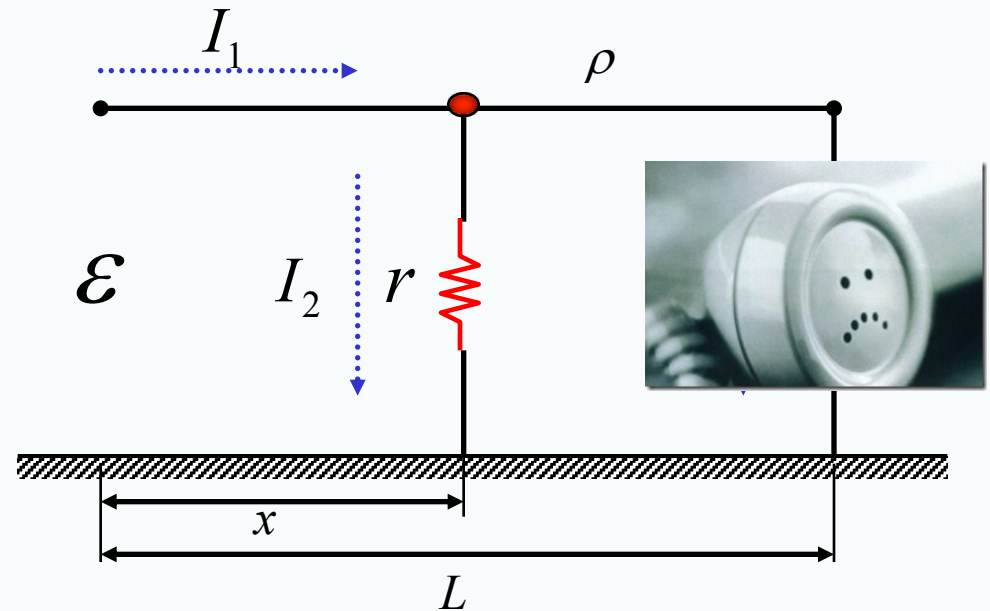

$$I_1 = I_2 + I_3$$

$$\mathcal{E} - x\rho I_1 - I_2 r = 0$$


$$I_2 r - (L - x)\rho I_3 = 0$$

$$\mathcal{E} = \left[ x\rho + \frac{x\rho r}{(L - x)\rho} + r \right] I_2$$

$$I_3 = \frac{\mathcal{E} r}{\rho(Lx\rho - x^2\rho - rL)}$$

$$x = \frac{L}{2}$$

# Simple circuits

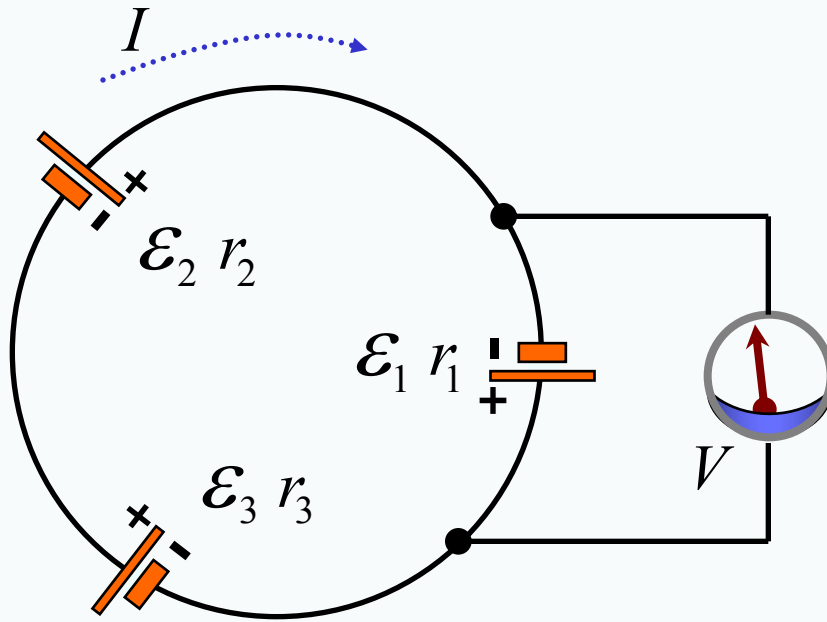

$$r_1 = r_2 = r_3 = 1 \Omega$$

$$\mathcal{E}_1 = 11V \quad \mathcal{E}_2 = \mathcal{E}_3 = 5V$$

$$\mathcal{E}_1 - Ir_1 + \mathcal{E}_2 - Ir_2 + \mathcal{E}_3 - Ir_3 = 0$$

$$I = \frac{\mathcal{E}_1 + \mathcal{E}_2 + \mathcal{E}_3}{r_1 + r_2 + r_3} = 7 \text{ A}$$


$$\Delta V_1 = -\mathcal{E}_1 + Ir_1 = -4 \text{ V}$$

$$\Delta V_2 = -\mathcal{E}_2 + Ir_2 = 2 \text{ V}$$

$$\Delta V_3 = -\mathcal{E}_3 + Ir_3 = 2 \text{ V}$$

$$\mathcal{E} = K \cdot r \quad \Delta V_i = -\mathcal{E}_i + Ir_i = -\mathcal{E}_i + r_i \frac{K \sum r_i}{\sum r_i} = 0$$

# Adding capacitor – steady state

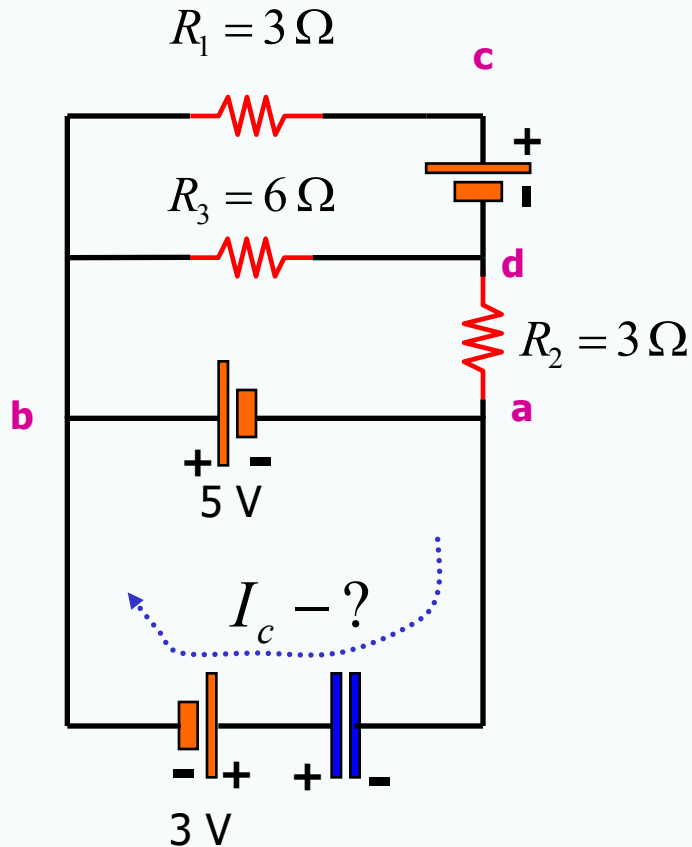

Polarity -?  $Q - ?$

Adding an open circuit does not affect currents in other parts of the circuit.

$$+\Delta V_c - 3\text{ V} - 5\text{ V} = 0$$

$$\Delta V_c = 8\text{ V}$$


$$Q = C\Delta V_c = 1\text{ }\mu\text{F} \cdot 8\text{ V} = 8\text{ }\mu\text{C}$$

---


$$-\Delta V_c + 3\text{ V} - 5\text{ V} = 0$$

$$Q = 2\text{ }\mu\text{C}$$

# Charging capacitor

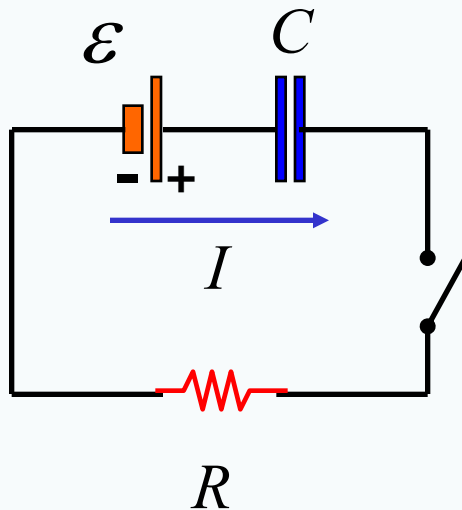

$$\mathcal{E} - \frac{q}{C} - IR = 0$$

$$t = 0: \quad \mathcal{E} - IR = 0$$

$$t = \infty: \quad \mathcal{E} - \frac{Q}{C} = 0$$

$$\mathcal{E} - \frac{q}{C} - \frac{dq}{dt} R = 0$$

$$q(t) = \mathcal{E}C \left( 1 - \exp\left\{ -\frac{t}{RC} \right\} \right) \quad I(t) = \frac{\mathcal{E}}{R} \exp\left\{ -\frac{t}{RC} \right\}$$

**Discharge:**

$$q(t) = \mathcal{E}C \exp\left\{ -\frac{t}{RC} \right\} \quad I(t) = -\frac{\mathcal{E}}{R} \exp\left\{ -\frac{t}{RC} \right\}$$



# To remember!

- **Electric current is charge passing through a given area per unit time.**
- **Current density in a conductor is proportional to the electric field.**
- **If a potential difference is maintained across a resistor, the power supplied to it will be equal to the product of the potential difference and the current.**
- **Real battery can be considered as an ideal one connected in series with a small resistance called internal resistance.**
- **For serial connection the resistance are summed; for parallel - their reciprocal values.**
- **When a closed-circuit loop is traversed, the sum in the changes of potential must be zero.**
- **At any junction the sum of inflowing current must be equal to the sum of currents flowing out.**



# To remember!

- **When a closed-circuit loop is traversed, the sum in the changes of the electric potential must be zero.**
- **At any junction the sum of the inflowing currents must be equal to the sum of the currents flowing out.**
- **No current flows through an open circuit, e.g. through capacitor.**
- **In non-steady state, however, transient currents can exist, e.g. during charging and discharging capacitors.**
- **The product  $RC$  is called the time constant of a circuit. It defines, e.g., rate of exponential loss of the charge by capacitor during its discharge.**

